



Name: \_\_\_\_\_,

ID: \_\_\_\_\_

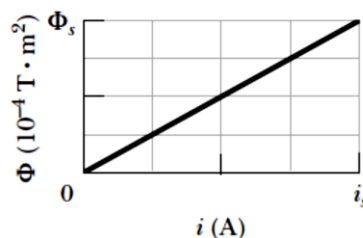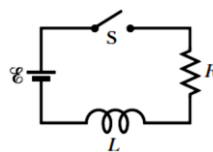**Q1)** In the left figure, the inductor has 25 turns and the ideal battery has an emf of 16 V. The right figure gives the magnetic flux  $\phi$  through each turn versus the current  $i$  through the inductor. The vertical axis scale is set by  $\phi_s = 4 \times 10^{-4} \text{ T}\cdot\text{m}^2$ , and the horizontal axis scale is set by  $i_s = 2.00 \text{ A}$ . If switch S is closed at time  $t = 0$ , at what rate  $di/dt$  will the current be changing at  $t = 1.5\tau_L$ ?

$$N\phi = Li$$

$$L = N \frac{\Delta\phi}{\Delta i} \Rightarrow L = 25 \times \frac{4 \times 10^{-4}}{2} = 5 \text{ mH}$$



$$i = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau_L}) \Rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-t/\tau_L}$$

$$\Rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-1.5} = \frac{16}{5 \times 10^{-3}} e^{-1.5} = 7.14 \frac{\text{A}}{\text{s}}$$

**Q2)** Two coils are at fixed locations. When coil 1 has no current and the current in coil 2 increases at the rate 15.0 A/s, the emf in coil 1 is 25.0 mV. (a) What is their mutual inductance? (b) When coil 2 has no current and coil 1 has a current of 3.60 A, what is the flux linkage in coil 2?



$$\mathcal{E}_{\text{ind}} = 25 \text{ mV} \quad \frac{di_2}{dt} = 15 \text{ A/s}$$

$$\Rightarrow \mathcal{E}_1 = -M \frac{di_2}{dt} \Rightarrow M = \frac{\mathcal{E}_1}{di_2/dt} = 1.67 \text{ mV}$$



$$i_1 = 3.6 \text{ A} \quad \mathcal{E}_{21}$$

$$N_2 \phi_{21} = M i_1 = 6.00 \text{ mWb}$$